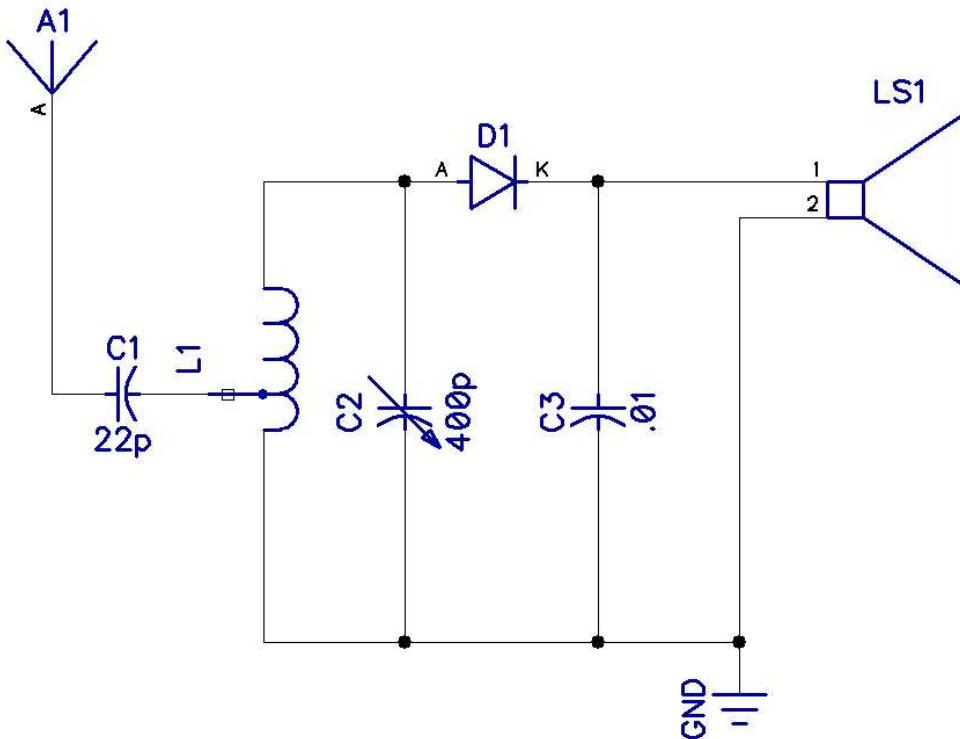



[Raspberry Pi](#)
[Arduino](#)
[DIY Electronics](#)
[Programming](#)
[Videos](#)
[Resources](#)

## HOW TO BUILD AN AM RADIO RECEIVER

Posted by Graham Lambert | DIY Electronics | 1 ●



In this article, we will first talk about radio frequencies and amplitude modulation. Then we will build three different AM radio receivers in order of increasing complexity. The first AM radio has no amplifier and only relies on resonance to create sound. The second AM receiver has a transistor amplifier, and the final AM receiver circuit uses an [LM386 amplifier chip](#).

**PCBWay**  
PCB Fabrication & Assembly

**ONLY \$5** for 10 PCBs

- ✓ 24-hour Build Time
- ✓ Quality Guaranteed
- ✓ Most Soldermask Colors:

Order now

### INTRODUCTION TO AM RADIO RECEIVERS


FOLLOW US

SUBSCRIBE

Get new tutorials sent to your inbox!

EMAIL ADDRESS

SUBSCRIBE

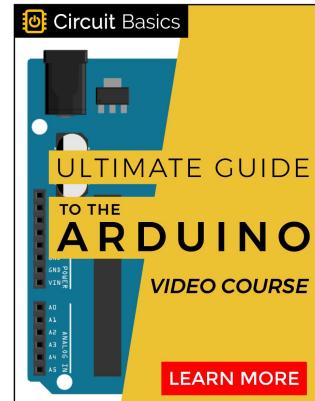

**PCBWay**

Professional  
**3D Printing**  
Start from **ONLY \$5**

Produces smooth, durable and accurate parts  
50+ Materials Available



**CNC Machining**  
Start from **ONLY \$50**


Machined prototypes in as fast as 1 day  
High-precision tolerances +/- 0.005" - 0.01"

 **Bạn thiết kế. Chúng tôi cung cấp.**

Những Sản phẩm Mới nhất cho những Thiết kế Mới nhất®




Medium wave and short wave were the main broadcast radio bands until the advent of FM. But they are still popular as they have more channel space than FM stations and offer longer range coverage, especially at night via the ionosphere. AM receivers are also simple and easy to build.



Radio stations in the medium wave and short wave bands transmit their signals using Amplitude Modulation (AM). This means that the transmitter radio (or carrier) signal is modulated with the music or speech content in a manner that the amplitude of the carrier is varied in relation to the incoming speech or music. AM is also used on all aircraft radios from 108 to 136MHz.
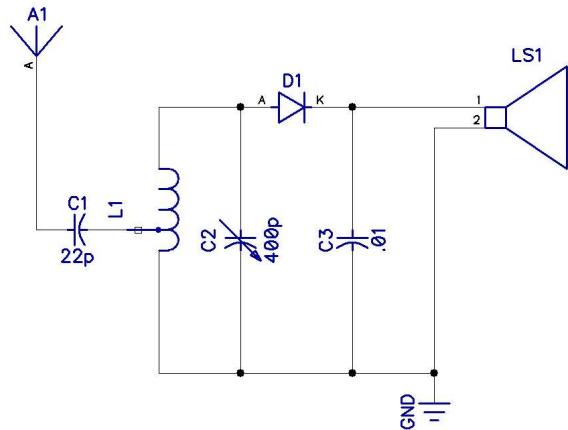
## HOW TO BUILD A SIMPLE AM RADIO

Shown below is a simple (and magical if you have ever built one) crystal radio circuit. Building this is an excellent start in understanding how AM radios work:




A crystal AM radio

The diode is ideally a [germanium diode](#), like the OA81, as it has a lower forward volt drop. But any diode will work, only with less volume. The LS is a high-impedance piezoelectric headphone like the [vintage 2000Ω "crystal earpiece"](#).

Capacitor C2 is a [variable capacitor](#) of about 300pF to 500pF.

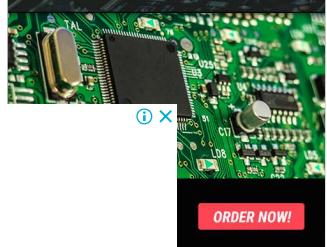INSTANT ONLINE TURN-KEY QUOTE AND ORDER IN MINUTES



**Bạn thiết kế. Chúng tôi cung cấp.**

Những Sản phẩm Mới nhất cho những Thiết kế Mới nhất®



[Learn more](#)

L1 is a coil wound on a ferrite rod with about 50 to 60 turns. The tap is at about 5 to 10 turns to be coupled to the antenna. Use [magnet wire](#) to wind the coil if possible.

For this radio work well, you will need a good earth connection and at least 20m of wire as high as possible outdoors as an antenna. What's truly amazing here is that this circuit will work without any batteries and provide hours of AM listening fun.

## HOW THE AM RADIO CIRCUIT WORKS

When the reactance (AC resistance) of capacitor C2 is the same as the reactance of the coil L1, resonance occurs at the frequency  $f=1/2\pi\sqrt{(LC)}$ .



For example, with L1 equal to 300 uH and C2 equal to 100 pF:

$$f = 1/2\pi\sqrt{(0.0003 H)(0.00000000001 F)} = 919\text{kHz}$$

If they are in parallel (as in our circuit), the combined impedance is very high, and if they are in series, resonance also occurs but the combined impedance is very low. The ratio of this dynamic impedance to any loss resistance present is called Q. The greater the Q, the more selective the circuit becomes.

This increase in selectivity enables the circuit to tune into the station you want. If the selectivity is low, you would hear other neighboring stations at the same time. (C1 is a small capacitor as well as the tap to prevent the antenna from damping the Q of the tuned circuit).

ⓘ ✕

The diode D1 rectifies and recovers the modulation and the capacitor C3 bypasses the radio (RF) part-leaving the original modulated audio. By changing the


**Bạn thiết kế. Chúng tôi cung cấp.**

Những Sản phẩm Mới nhất cho những Thiết kế Mới nhất®


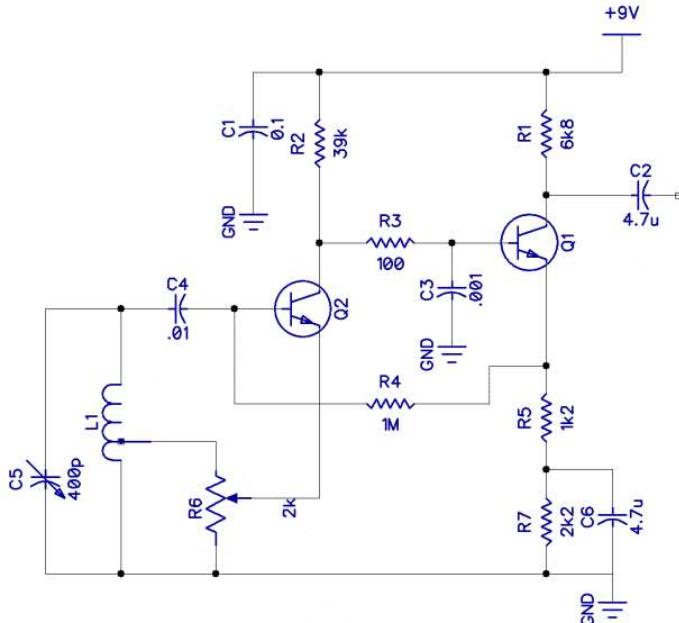
## TRANSISTOR AMPLIFIED AM RADIO


Before the advent of easy-to-use amplifier IC's such as the LM386, receivers were made from designs using discreet components. A popular choice was the regenerative receiver shown below.




A two-transistor regenerative receiver

Rectification of the AM signal takes place inside Q2, and R3. Transistors Q1 and Q2 can be any NPN transistor. Capacitor C3 removes any remaining RF components. Some of the demodulated signals are fed back as positive feedback through R4 into the tap of L1 via the regeneration control R6. This will have the effect of starting to oscillate. The idea is to adjust potentiometer R6 to a point where oscillation is about to start and back off a bit. This has the effect of greatly increasing the sensitivity and selectivity of the receiver. R5 generates some negative feedback, which improves the audio quality.

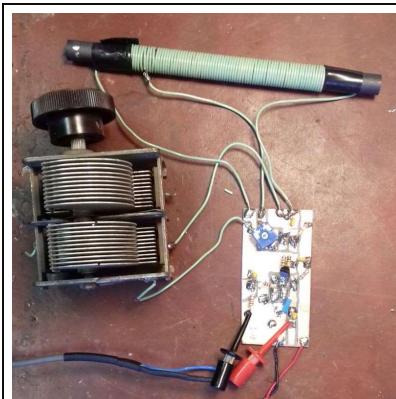Variable capacitor C5 and coil L1 are the tuned circuit. Coil L1 is 60 turns on a 1 cm diameter ferrite rod (about 300uH) with 5 turns added for the tap. In the [prototype board](#) below, I am only using one half of the variable capacitor.



Regenerative radio breadboard

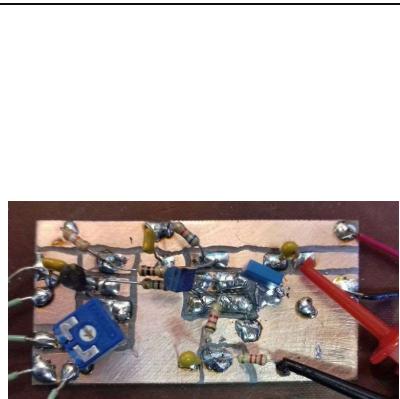


Close up of the PCB

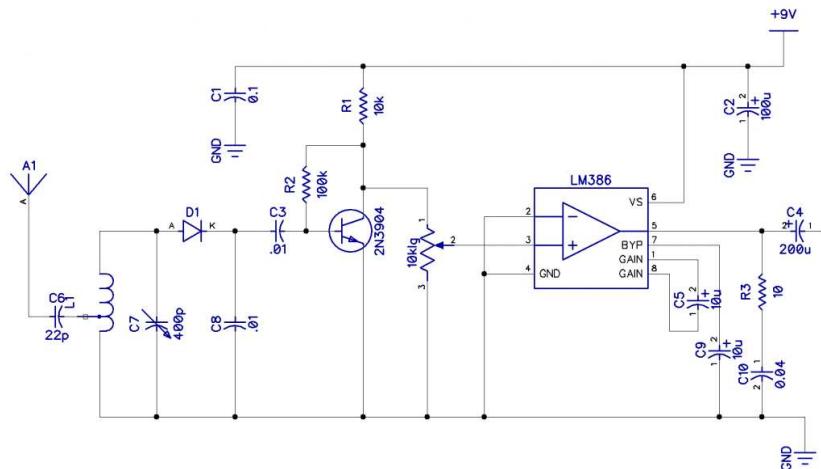**Bạn thiết kế. Chúng tôi cung cấp.**

Những Sản phẩm Mới nhất cho những Thiết kế Mới nhất®



to work without an antenna or a good earth connection. Also, the LM386 provides enough amplification power to drive a small speaker.




AM radio with LM386 amplifier

Capacitors C5 and C9 set the overall gain of the LM386. If you find the gain too high, you can adjust it following the instructions in our article on how to [Build a Great Sounding Audio Amplifier \(with Bass Boost\)](#). The article also discusses how to tweak an LM386 amplifier circuit to get better sound.

**Resistor** R3 and capacitor C10 prevent unwanted instability of the LM386's output by providing a known load at frequencies above audio.

	2 IN 1 8CH Network Ethernet RS485 Relay Modbus RTU Slave TCP/IP UDP UART Switch Module PLC Industrial Control Board	\$13.99
		\$8.99
\$21.99		\$102.99
	<a href="#">More Info</a>	

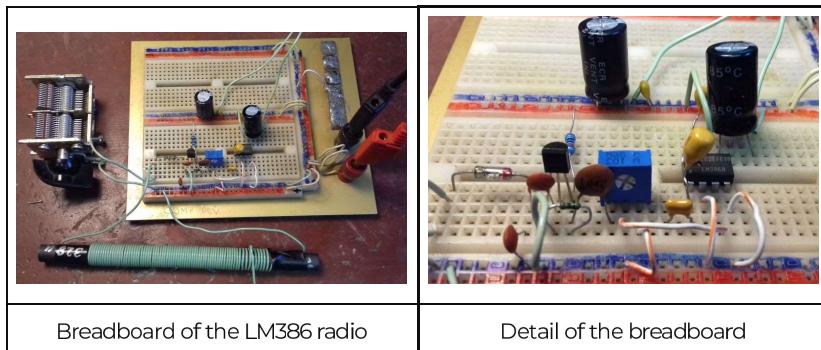The [2N3904 transistor](#) provides a moderately high impedance to the tuned circuit giving good selectivity.



In conclusion, making your own AM receiver can be easy and gives a lot of rewarding listening pleasure. All of the above circuits were built and tested and

**Bạn thiết kế. Chúng tôi cung cấp.**

Những Sản phẩm Mới nhất cho những Thiết kế Mới nhất®




make one by gluing drum paper to two sheets of A4 paper and connect them...

with crocodile clips. Sliding one sheet over the other makes a variable cap provided they don't make electrical contact.




If you don't want to go through the process of sourcing all of the parts for building these AM radios, there are some really cool [DIY radio kits on Amazon](#).

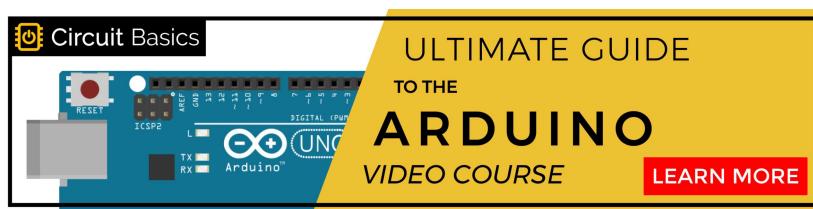Thanks for reading and be sure to leave a comment below if you have questions about anything!




SHARE: [f](#) [t](#) [g+](#) [p](#) [m](#)

## RELATED POSTS

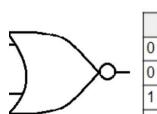


A	E
0	0
0	1
1	0
1	1


[Introduction to Digital Logic Chips](#)

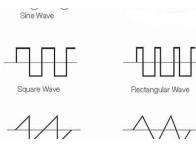

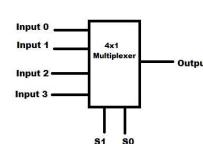[How to Build a Sawtooth and Triangle Wave Generator](#)



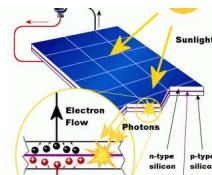[A Complete Guide to Electronic Multiplexers](#)



[How to Build a Solar Powered Battery Charger](#)

## 1 COMMENT

Erik van Zijst on March 28, 2022 at 7:54 am

**Bạn thiết kế. Chúng tôi cung cấp.**

Những Sản phẩm Mới nhất cho những Thiết kế Mới nhất®



is wrong in that there's too many zeros. 100pF is 0.000,000,000,1 (not 0.000,000,000,001).

REPLY

## LEAVE A REPLY

Your email address will not be published. Required fields are marked \*

COMMENT

NAME \*

EMAIL \*

WEBSITE

- Save my name, email, and website in this browser for the next time I comment.
- Notify me of follow-up comments by email.
- Notify me of new posts by email.

For security, use of Google's reCAPTCHA service is required which is subject to the Google [Privacy Policy](#) and [Terms of Use](#).

[I agree to these terms.](#)

POST COMMENT

^

---

---

**Bạn thiết kế. Chúng tôi cung cấp.**

Những Sản phẩm Mới nhất cho những Thiết kế Mới nhất®



Discover the solutions that enable your innovation with our experts.

STMicroelectronics

Learn More

Copyright **Circuit Basics**

Raspberry Pi Arduino DIY Electronics Programming Videos Resources About Contact Us Privacy Policy [f](#) [t](#) [g](#) [y](#)